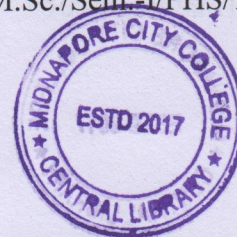


**PG (NEW) CBCS**  
**M.Sc. Semester-I Examination, 2018**  
**PHYSICS**  
**PAPER: PHS-195**  
**(PRACTICAL)**

**Full Marks: 50****Time: 3 Hours**

**PHS 195: ELECTRONICS PRACTICAL –I**

The questions are of Equal Value

[Experiment: 35, LNB: 5, Viva Voce: 10]

Theory/working formula .....	5
Circuit diagram and design of the circuit .....	5
Implementation .....	4
Data recording .....	10
Drawing the graphs and calculations .....	7
Accuracy .....	4

1. Design a LC filter circuit having specified cut-off frequency and study the frequency response characteristics. Draw the frequency response curve and find the cut-off frequency and compare with theoretical value.
2. Implement a circuit to study the drain and transfer characteristics of a FET and find out the drain resistance, mutual conductance and amplification factor of the FET.
3. Design and implement a 2 bit Comparator circuit and verify its truth table.
4. Design and implement a JK/MS flip-flop using NAND gates only and verify the truth table.
5. Implement on inverting OPAMP circuit for a particular gain (to be specified by the examiners) and study its linearity and frequency response characteristics. Find out its bandwidth.
6. Implement on non-inverting OPAMP circuit for a particular gain (to be specified by the examiners) and study its linearity and frequency response characteristics. Find out its bandwidth.
7. Study a step up and step down transformer and measure following parameters of the circuit
  - a) Primary inductance
  - b) Secondary inductance
  - c) Mutual inductance
  - d) Turn ratio
  - e) Coupling constant