

Second Semester Examination-2018

M.Sc. PHYSICS

Paper Code: PHS 203

Full Marks : 40

Time: 2 Hours

Use Separate scripts for Group A & Group B


Group A

(Analog Electronics-II)

Answer Question no 1 and any One from the rest.

1. Answer any five the following: 2×5=10

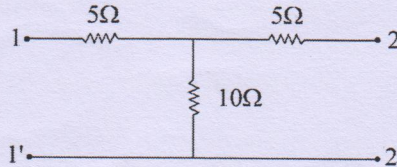
a. Find the characteristic impedance of the following T – network.



- b. Is it possible to design a constant – k filter (Ray-LPF) using capacitors or inductors only? Why?
- c. Suppose your transmission line is open ended. Find the value of the reflection coefficient and Voltage Standing Wave Ratio (VSWR).
- d. Why a photo transistor is more sensitive than a photo diode?
- e. Define hybrid parameters of a two port network.
- f. Draw the cross sectional diagram of a disc and its IV characteristics.
- g. Show that an ideal transmission line is distortion less line.

2.a. Explain how a given T- network can be converted into its equivalent π network with necessary derivations. 5

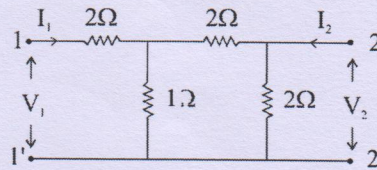b. Find out the hybrid parameters of the following circuit. 5



3.a. Obtain the expression of Voltage and current equations of a transmission line.

- b. Using the above equations find also the expression of reflection coefficient of the line. 2
- c. Describe the principle of operation with a proper circuit diagram of a band-pass filter. 4

or

Design a constant K high pass filter having cut-off frequency of 10kHz and derive the expression for cut off frequency.

Group B

(Digital electronics-II)

Answer Question no 1 and any One from the rest.

1. Answer any five of the following: 5×2=10
- Design a half adder circuit using 4:1 MUX.
 - Define settling time & resolution.
 - Design a one bit comparator.
 - What are the advantages of digital communication over analog communication?
 - What are positive & negative logic.
 - What is volatile & non-volatile memory?
 - What is aliasing effect & how it can be overcome.
- 2.a. Explain steps and timing of data flow using timing diagram when instruction code (MOVC, A – 4F_H) stored in a location 8005H is fetched in case of 8085 microprocessor. 6
- b. What is sampling theorem? Discuss different techniques of sampling. 1+3
- 3.a. State the working principle of any one ADC system with proper block diagram. 3
- b. Construct 512×4 bit memory using two 256×4 bit PROM. 2
- c. Store the following two outputs in a single FPLA memory circuit 3
- $$X = \overline{AB} + A\overline{B}$$
- $$Y = AB + \overline{A}\overline{B}$$
- d. Show how to solve the equation 2
- $$Y = \overline{ABC} + \overline{A}BC + A\overline{B}\overline{C}$$
- by using 8:1 multiplexer IC.