

PG (NEW) CBCS
M.Sc. Semester-I Examination, 2019
PHYSICS
PAPER: PHS-104

Full Marks: 40**Time: 2 Hours****Write the answer for each unit in separate sheet**

The figures in the right-hand margin indicate full marks.
 Candidates are required to give their answers in their own words as far as practicable.

PHS 104.1: ANALOG ELECTRONICS - I**Marks: 20**

1. Attempt any two of the following: (2 × 2 = 4)
 - a. What is Vestigial Side Band (VSB) modulation and where it is used?
 - b. What is duplexer and where it is used?
 - c. What is slew rate of an OP-AMP? For an ideal OP-AMP, what should be its value?
 - d. What is secant law for sky-wave propagation?
2. Attempt any two of the following: (4 × 2 = 8)
 - a. How you can create current to voltage converter using OP-AMP?
 - b. Show that for ionospheric wave, the refractive-index of the ionised medium is given by $n = \sqrt{1 - \frac{81N}{f^2}}$, where $e = 1.6 \times 10^{-19} \text{ C}$, $m = 9.1 \times 10^{-31} \text{ kg}$ and $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$.
 - c. Draw the circuit diagram of a balanced modulator and explain with necessary derivation, how it can generate DSB-SC signal?
 - d. (i) Find the BW of the channel required to transmit an FM signal with $\Delta F = 75 \text{ KHz}$ and maximum frequency of the modulating signal = 15 KHz.
 (ii) A differential amplifier has $\text{CMRR} = 100 \text{ dB}$. Its differential mode gain is 10,000. Find its common mode gain.
3. Attempt any one of the following: (8 × 1 = 8)
 - a. What do you mean by amplitude modulation? Draw a circuit using BJT which generates AM modulated signal. Draw the block diagram of a Superhetrodyne FM radio receiver. (2+3+3)
 - b. i) Derive radar range equation and explain how the radar range can be increased? (5)
 ii) Explain how the distance of a fixed target can be found out by using two frequency CW radar. (3)

(Turn Over)

(2)

PHS 104.2: DIGITAL ELECTRONICS - I**Marks: 20**

1. Answer any two of the following: (2 × 2 = 4)
- Draw a 8:1 MUX using two 4:1 MUX.
 - Convert the clocked D FF into a JK-type FF.
 - Simplify using K map $f(a,b,c,d) = \sum_m(0,1,9,12,13,14,15) + d(4,5,8,9)$
 - Draw the waveforms to shift the binary number 1010 into the serial-in and serial-out shift register.
2. Answer any two of the following: (4 × 2 = 8)
- Design a 4-bit ripple carry Adder.
 - Design a full adder circuit using 4:1 MUX.
 - Draw the K-map for the function F and minimise the function F' in sum of product form (a) $F = W'X'YZ + WYZ$ (b) $F = A'B'C'D' + A'CD + ABCD$
 - Design a MOD-10 counter. Also draw the timing waveforms.
3. Answer any one of the following (8 × 1 = 8)
- Design a BCD to 7 segment decoder circuit.
 - i) In an astable multivibrator $R_A = 2.2k\Omega$, $R_B = 3.9k\Omega$ and $C = 0.1 \mu F$ (R_A & R_B are charging resistor and discharging resistor). Determine the positive pulse width t_c , negative pulse width t_d and free running frequency f_0 . What is the duty cycle of the output waveform? (4)
 ii) A digital system receives 4 bit binary numbers. Design a display system to display only the BCD numbers 0 to 9 and for non-BCD numbers the display should show the figure of English alphabet E which indicates error. (4)
