

Total pages: 2

PG CBCS
M.SC. Semester-I Examination, 2021
DEPARTMENT OF PHYSICS
PAPER: PHS 104
(APPLIED ELECTRONICS)

Full Marks: 40**Time: 2 Hours****Write the answer for each unit in separate sheet****PHS 104.1****Answer any TWO questions of the following:****2X10=20**

1. (a) What is the use of OP-AMP in open-loop configurations? Explain inverting and non-inverting comparator (zero reference voltage) with proper circuit diagram and transfer characteristics. (1+4)
- (b) Design a OP-AMP Integrator and derive its output voltage expression in terms of input voltage? What will be the output wave form of the above circuit if we input a square waveform? (4+1)
2. (a) Describe n-MOSFET and p-MOSFET for both enhancement and depletion mode operation using proper schematic and electrical characteristics (5)
- (b) Derive the expression for the radiation resistance of a half wave antenna. (5)
3. (a) What is dipole antenna? Derive the expression of radiation pattern of an half wave antenna? (1+5)
- (b) What is Active Filter? What is the Butterworth response of an active filter? (1+2)
4. (a) Neglecting the effect of earth's magnetic field and the energy loss, show that the refractive index of the ionosphere is given by,

$$n = \sqrt{1 - \frac{80.8N}{f^2}}, \text{ where } N = \text{no. of electrons/cc. } f = \text{frequency in kHz} \quad (5)$$
- (b) Why modulation is necessary in communication, explain in details. What is the advantages of FM over AM? (3+2)
5. (a) Derive RADAR range equation and explain how radar range can be increased? (5)
- (b) What is the need of duplexer in a RADAR system? Describe Doppler Radar? (1+4)

(P.T.O.)

(2)

PHS 104.2**Answer any TWO questions of the following:****2X10=20**

1. (a) Simplify the boolean expression $F \equiv \overline{A}BC + A\overline{B}C + ABC$ using (i) Sum of minterms.
(ii) Sum of Maxterms. (3+3)
- (b) Realize the above simplified boolean expression using NAND-NAND and NOR-NOR Logic gates. (2+2)
2. (a) What is sequential circuit? Draw a diagram of a JK master slave flip-flop and describe its operation. (1+5)
- (b) Show how a SR Flip-Flop can be converted to JK Flip-Flop? (4)
3. (a) What is shift register? What is universal shift register You have 2 bit parallel data. How can you transform it in serial form? (1+1+3)
- (b) Design a bi-directional 3-bit shift register. (5)
4. (a) What is counter? Design a synchronous counter which has only (00) and (10) states. (1+4)
- (b) Design a MOD-2 counter and draw output wave-form.
5. (a) What do you mean by bi-stable, mono stable and astable multivibrator? Design a bi-stable multivibrator with 555 timer with a proper circuit diagram. (2+5)
- (b) Give the schematic idea of 7 segment display system. (3)
