

Total page: 1

PG CBCS
M.Sc. Semester-II Examination, 2021
PHYSICS
PAPER: PHS 295
(ELECTRONICS PRACTICAL-II)

Full Marks: 50

Time: 3 Hour

Answer any TWO questions from the following:

2×25=50

1. Describe how you can design a 4 bit ripple up/down counter and develop different modulo counters from it.
2. Describe necessary theory to design a 4 bit Ring counter and a Twisted Ring counter.
3. Describe how you can study a differential amplifier circuit using OP-amp and find out its transfer characteristics and differential mode gain.
4. Design a window comparator using Op-amps and describe how you can study its characteristics.
5. Describe necessary theory of a Monostable multivibrator with timer IC 555.
6. Describe how you can determine the slew rate of an Op-amp.
