

Total pages: 2

PG CBCS
M.SC. Semester-III Examination, 2021
PHYSICS
 PAPER: PHS 303B (SPL PAPER)
 (APPLIED ELECTRONICS)

Full Marks: 40

Time: 2 Hours

Write the answer for each unit in separate sheet

The figures in the right-hand margin indicate full marks.
 Candidates are required to give their answers in their own words as far as practicable

PHS 303B.1

Marks: 20

Answer any TWO questions of the following:

2X10=20

1. (a) Draw proper circuit diagram of a Logarithmic Amplifier with a transistor. Derive the output voltage expression in terms of input voltage. 1+3
- (b) Draw proper circuit diagram of analog multiplier and derive the output voltage expression in terms of input voltage. 2+4
2. (a) Explain the working principles of inverting Schmitt trigger with necessary derivation. Why it is called bi-stable multi-vibrator? 4+1
- (b) What is Schmitt trigger oscillator? Derive the general expression for the time period of oscillation. 1+4
3. (a) What is Instrumentation Amplifier. Draw the proper circuit diagram of an Instrumentation Amplifier. Derive the output voltage expression. 1+2+4
- (b) What is Active Filter? What is the Butterworth response of an active filter? 1+2
4. What is Voltage controlled Oscillator? What is its advantage over a LC tuned oscillator? What is Phase locked loop and explain its operation 2+3+5
5. (a) Draw the circuit diagram of regulated power supply using OP-AMP as comparator, a power transistor and current limiter. Explain its operation and derive the output voltage expression. 2+3
- (b) Draw the circuit diagram of peak detector using OP-AMP and explain its operation. 5

(P.T.O.)

(2)

PHS 302B.2**Marks: 20****Answer any TWO questions of the following:****2X10=20**

1. (a) What is advantages and disadvantages between TTL and CMOS Logic Circuits? 3
 (b) What is Noise immunity, Fan-in and Fan-out of digital logic. 3
 (c) Draw CMOS inverter circuit and explain its operation. 4
2. (a) Differentiate SRAM and DRAM. 4
 (b) Draw unit cell structure of SRAM and DRAM and explains its Operations. 6
3. (a) What is Ratioed and Ratio less Shift Registers? 4
 (b) Draw 2 phase ratioed logic circuit diagram and explain its operations. 6
4. (a) Define briefly TCP/IP and FTP protocol. 4+3+3
 (b) What is FDMA and CDMA
 (c) What is the basic difference between 2G and 3G system in mobile communication?
5. (a) Give the truth table for binary to BCD converter. 3
 (b) Give 4:2 Encoder circuit. 3
 (c) Solve the following equation by 8:1 MUX IC 4

$$Y = \sum_m (0, 3, 5)$$
